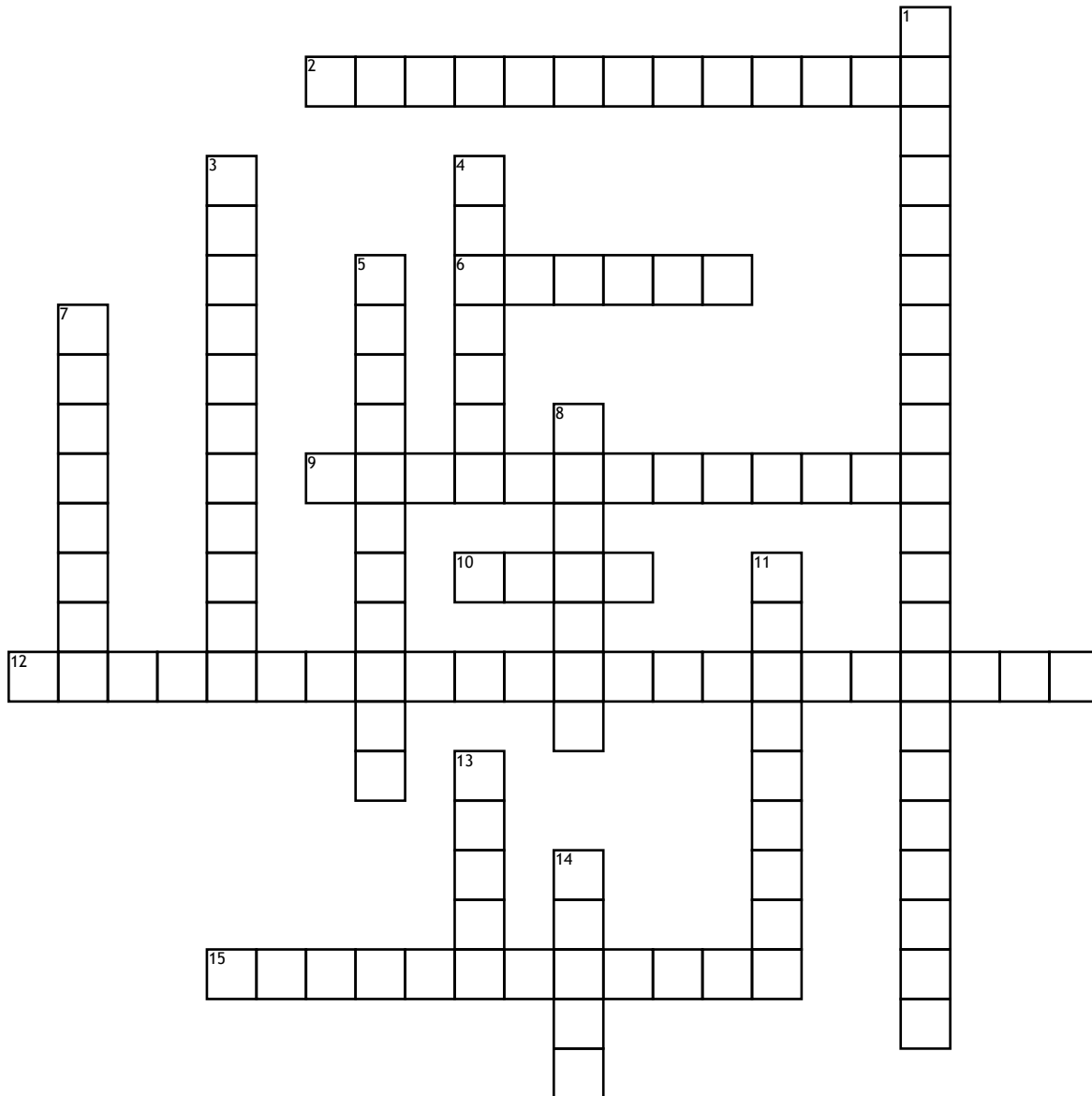


Digital Logic and Designs (CSE1003)



Across

- 2. A sequential circuit where only the first flip-flop is clocked by an external clock.
- 6. Asynchronous counters are often called _____ counters.
- 9. the circuit can go into the wrong state depending on slight differences in the propagation delays of the gates which is known as _____.
- 10. A universal gate
- 12. A fixed architecture logic device with programmable AND gates followed by programmable OR gates.

15. A ripple counter is an _____ counter.

Down

- 1. It has programmable AND array and fixed OR array.
- 3. A sequence of equally spaced timing pulses may be easily generated by a(n) _____.
- 4. Output is high, when any one of the input is high
- 5. Helpful to simplify Boolean expressions with limited inputs
- 7. A group of flip flop which holds the binary information

8. A sequential circuit which is used to display the number of time any event is repeated or happening.

- 11. The sequential Circuits are designed using the combinational circuits along with a memory devices known as _____.
- 13. The _____ do not have clock input but flip flop has a clock input
- 14. Asynchronous sequential circuits do not use _____ signals as synchronous circuits do.